

Lab Task:

Question 01:

Using K-MAP, write down minimum SOP and actual expression for each case. Create Truth Table of Actual expression and implement Both actual and reduced expression on Logisim.

1.

AB \ C	0	1
00	1	
01		1
11	1	1
10		

Actual

$$\bar{A}\bar{B}\bar{C} + \bar{A}BC + ABC + AB\bar{C}$$


Reduced

$$\bar{A}\bar{B}\bar{C} + BC + AB$$


A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Q1 part 1

Actual

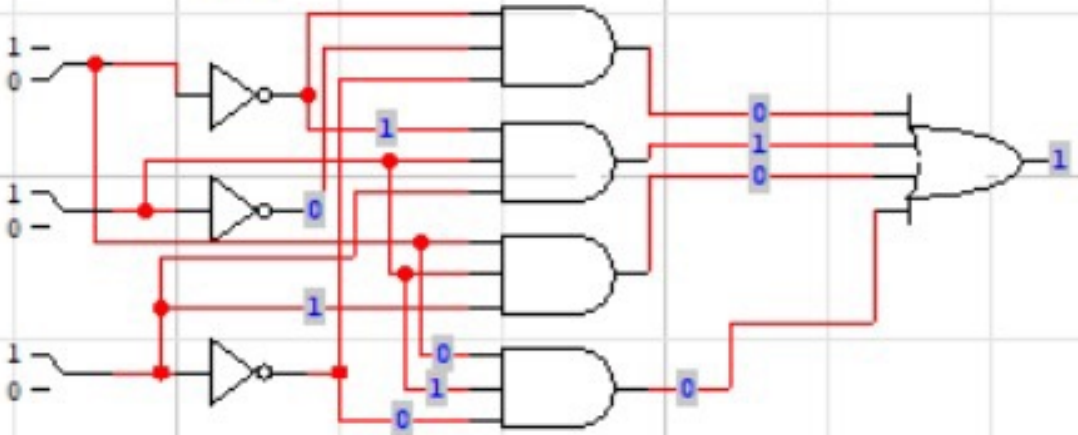

Simplified

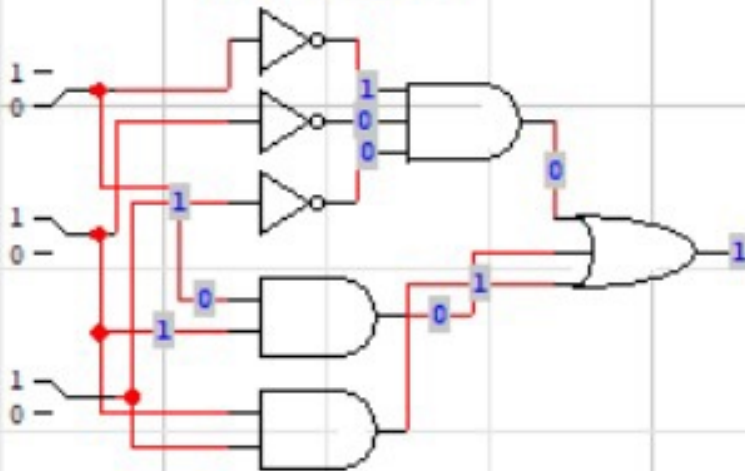

2

		C	
AB		0	1
00		1	1
01		1	
11			1
10		1	1

Actual

$$\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C$$


Reduced

$$\bar{B} + \bar{A}\bar{C} + AC$$


A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Q1 part 2

Actual

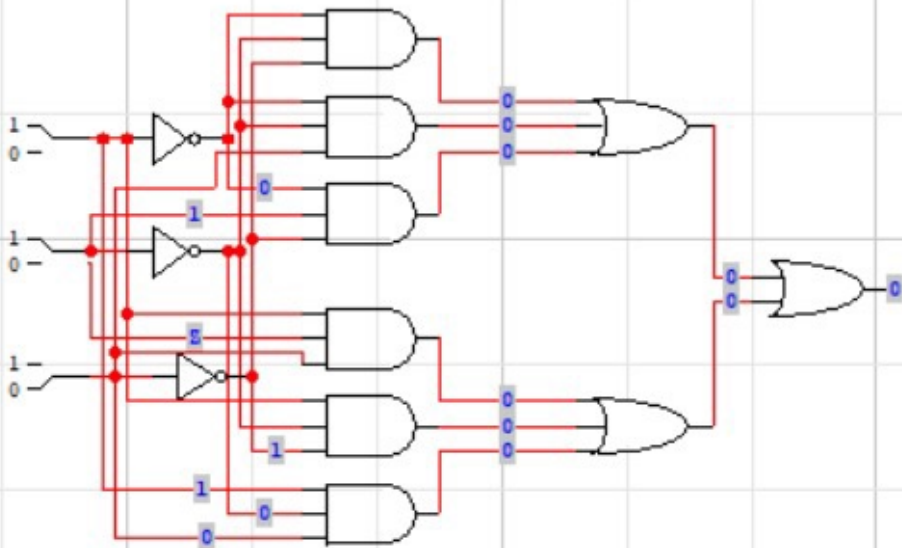

Simplified

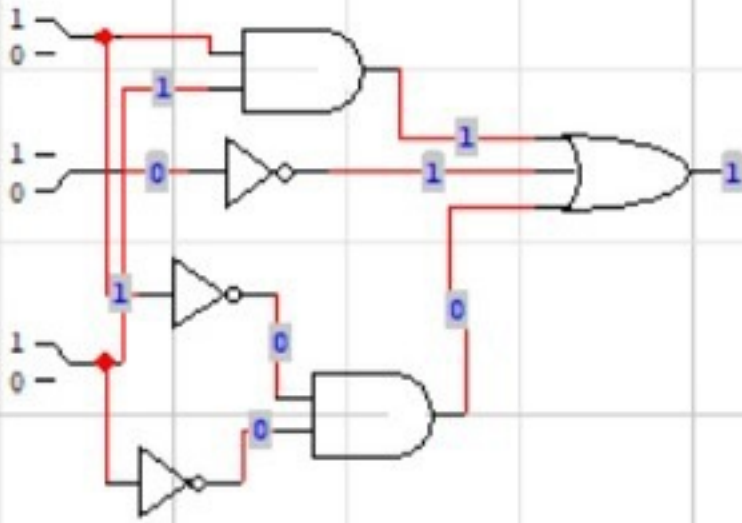

Question 02:

Make a POS Simplified Expression of the following. Note the Blank spaces represent 0.

1.

		CD			
		00	01	11	10
AB	00	1	1	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	0	1	1	0


Actual

$$\begin{aligned} & (A + B + \bar{C} + D)(A + B + \bar{C} + \bar{D}) \\ & (\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + C + \bar{D}) \\ & (\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + \bar{C} + D) \\ & (\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + \bar{C} + \bar{D}) \end{aligned}$$

Reduced

$$(\bar{A} + \bar{D})(A + B + \bar{C})(\bar{A} + \bar{B})$$

A	B	C	D	X
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

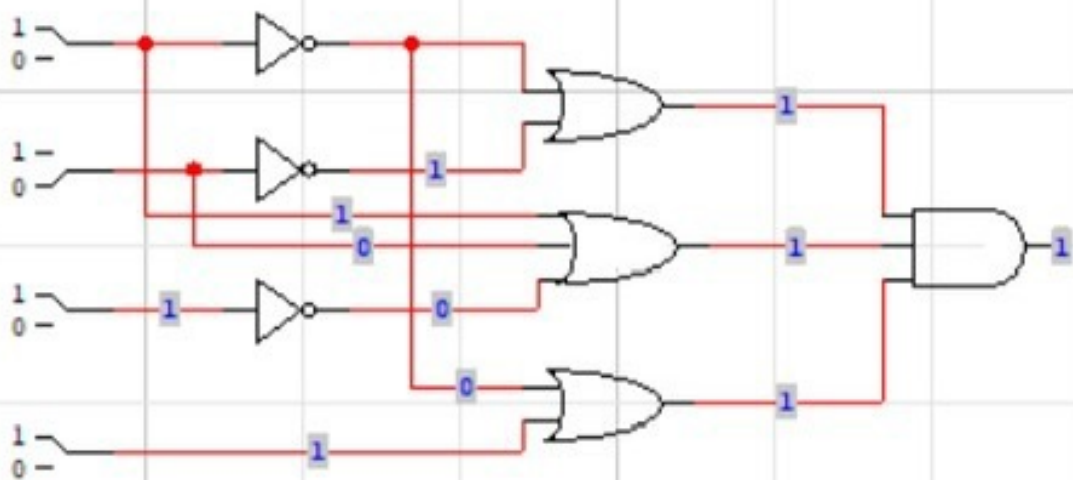

2.

CD \ AB		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	1	1	0	1
	11	1	1	0	1
	10	1	0	1	1


Actual

$$\begin{aligned}
 & (A + B + C + \bar{D})(A + B + \bar{C} + \bar{D}) \\
 & (A + \bar{B} + \bar{C} + \bar{D})(\bar{A} + \bar{B} + \bar{C} + \bar{D}) \\
 & (\bar{A} + B + C + \bar{D})
 \end{aligned}$$

Reduced

$$\begin{aligned}
 & (B + C + \bar{D})(A + B + \bar{D}) \\
 & (\bar{B} + \bar{C} + \bar{D})
 \end{aligned}$$

A	B	C	D	X
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

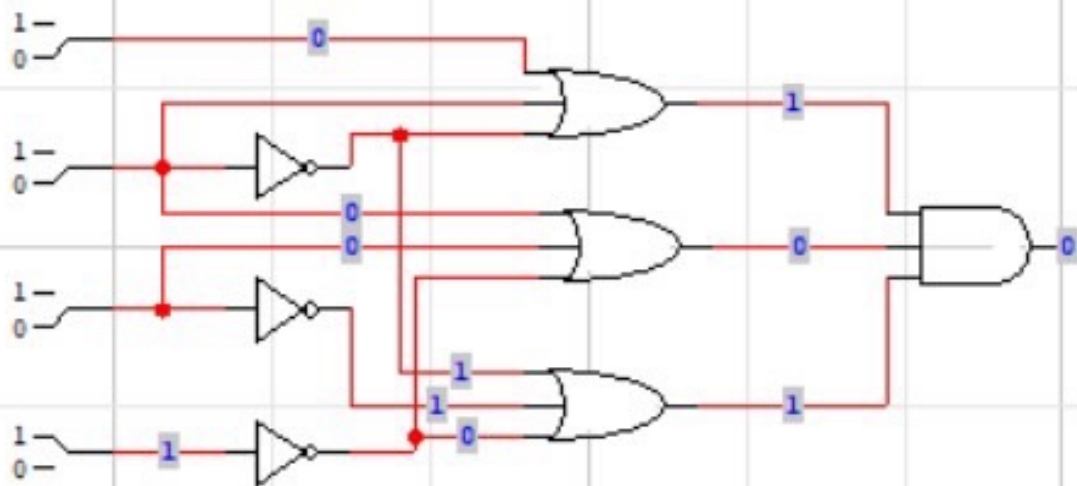

Question: 3 Use K-MAP to minimize the given SOP expression. Implement the minimized SOP on Logisim and Complete Truth Table.

$$\overline{A}\overline{B}C + \overline{A}BC + \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C}$$

$$\overline{A}\overline{B}C + \overline{A}BC + \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C}$$


101 011 001 000 100

AB \ C		
	0	1
00	1	1
01		1
11		
10	1	1

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

Simplified

$$\overline{B} + \overline{A}C$$

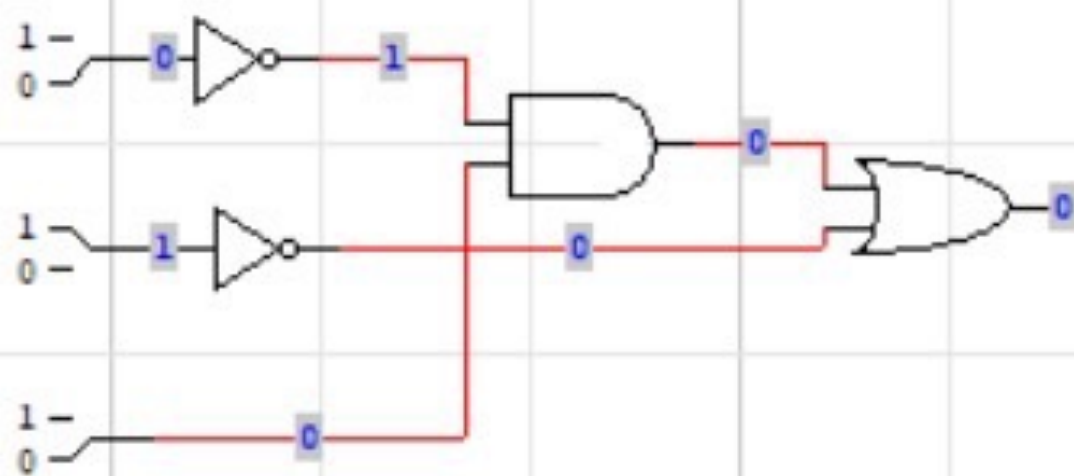

Question: 04 Use K-MAP to minimize the given SOP expression. Implement the minimized SOP on Logisim and Complete Truth Table. Also verify if and POS expression can be made using the derived K-Map if yes Built one and its circuit on the software.

$$A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D}$$

Actual

$$\begin{aligned} &A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} \\ &+ \bar{A}\bar{B}C\bar{D} + A\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} \\ &+ A\bar{B}C\bar{D} + A\bar{B}C\bar{D} \end{aligned}$$

AB \ CD	00	01	11	10
00	1	0	1	1
01	1	0	0	1
11	1	0	0	1
10	1	0	1	1


Simplified

$$\bar{D} + \bar{B}C \quad (\text{SOP})$$

$$(C + \bar{D})(\bar{B} + \bar{D})(\text{POS})$$

A	B	C	D	X
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

SOP

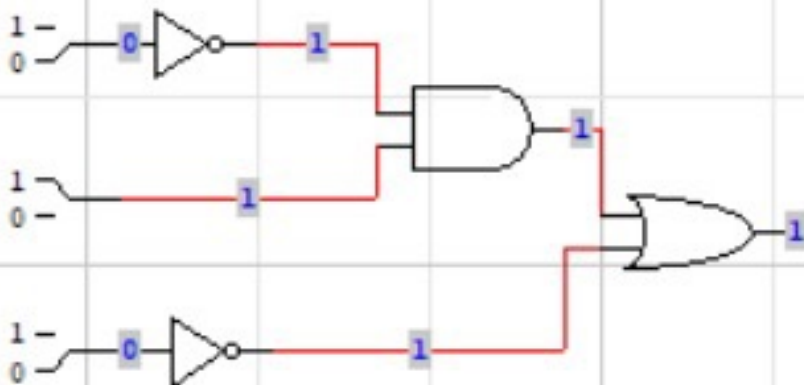

POS

